

## BAL vs. BALH and Microwave Black Magic

What is the difference between the BAL line of products ([BAL-0003/6/9SMG](#) and [BAL-003/6/10](#)) and the equivalent BALH products ([BALH-0003/6/9SMG](#) and [BALH-0003/6/10](#))?


Which one is a 1:1 (50  $\Omega$  single ended to 50  $\Omega$  differential/25  $\Omega$  single ended) transformer and which one is a 1:2 (50  $\Omega$  single ended to 100  $\Omega$  differential/50  $\Omega$  single ended) transformer?

The first question is easy to answer, the second not so much. Both product lines are based on a transmission line transformer (as described in our [Balun Basics Primer](#)), and in fact the same transmission line transformer core.

The surface mount and connectorized parts have different transmission line transformer cores, but the BALH and BAL have the same transmission line transformer in each version. This transmission line transformer is inherently a 1:1 construction. Since the transmission line is 50  $\Omega$  throughout, the output is 50  $\Omega$  differential/25  $\Omega$  single ended.

In the BALH series there is nothing but the transmission line transformer.

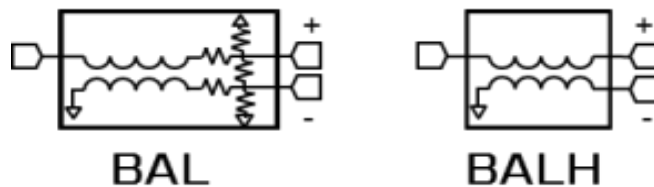In the BAL series, the transmission line transformer is resistively terminated on the differential side to create a good 50  $\Omega$  single ended/100  $\Omega$  differential match. The cost is 3 dB of extra insertion loss.



So far so good, but here is where it gets complicated:

*We have no way to make measurements of a 25 $\Omega$  component.*

Our VNAs, cables, connectors, and calibration kits are all 50  $\Omega$ . Since we cannot measure 25  $\Omega$ , we measure the BALH in a 50  $\Omega$  environment, and the results are still pretty good!

As an example, let's look at the BALH-0006SMG vs. the BAL-0006SMG. The balance is dictated by the core, and not really affected by the resistive matching, so let's just look at the insertion loss and return loss of the [BALH-0006SMG](#) measured in a 50 $\Omega$  environment:

---



更多信息，请联系我们：

地址：上海市普陀区中山北路 2911 号中关村科技大厦 1206 室

Tel: 137 6444 1515, Fax: 021-5291 8556



[www.fulai-elec.com](http://www.fulai-elec.com)

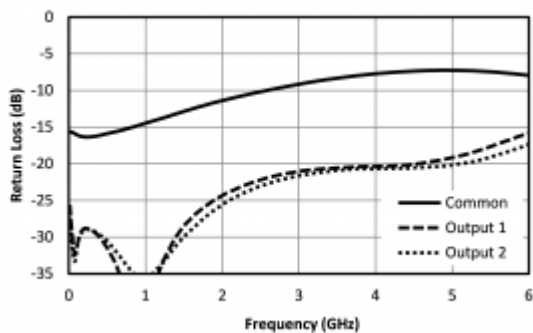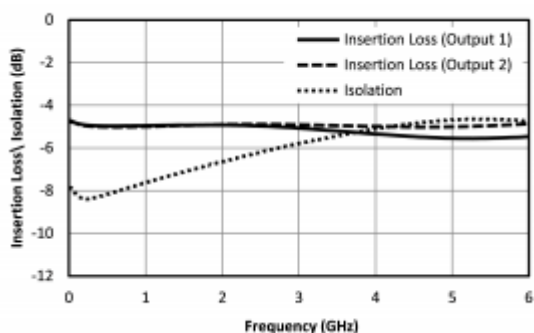Email: [sales@fulai-elec.com](mailto:sales@fulai-elec.com)



As you see the total insertion loss is the expected 3 dB split loss plus 2 dB of excess insertion loss, as expected. What is unexpected is the return loss. The differential port return losses (labeled as 'Output 1/2' assuming single ended to differential operation) are *much* better than you would expect if they were truly 25  $\Omega$  ports. The common port return loss is also better than you would expect if you were terminating a simple reactive T in a 100  $\Omega$  differential load. You would expect all three return losses to be 3 dB, and instead they are much better.

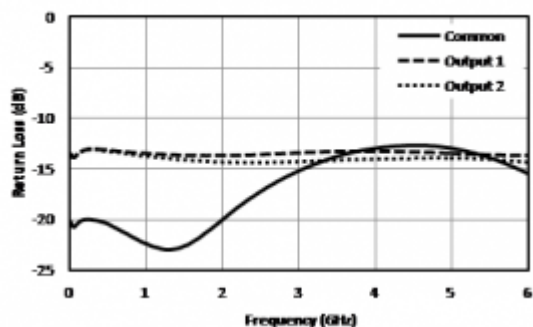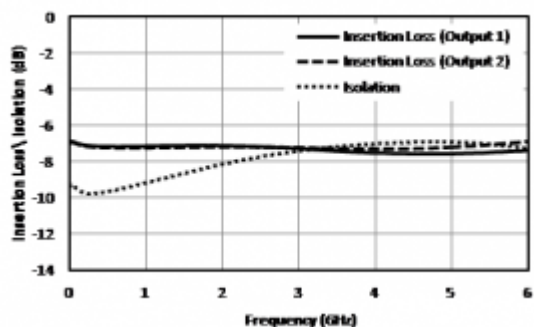Now look at the same data for [BAL-0006SMG](#)



As expected the insertion loss is a little less than 3 dB worse. The differential port return losses are a little worse, but the single ended return loss is significantly better, up to 5 db at the high end where it really starts looking rough for the BALH.

So in conclusion, I don't think that it is fair to say that the transmission line transformer, and therefore the BALH, is a **true** 1:1 transformer. There is obviously some type of impedance up-transformation going on, maybe not all the way to 100 ohm differential, but somewhere in the middle. That is why I think of the impedance in these baluns as 'squishy', almost quantum. When we do experiments with our 50 $\Omega$  equipment to try to tease it out, it resists our efforts.

For your purposes, you really just need to review the datasheets, make your best guess about your impedance environment, and test it out. Microwave Black Magic at it's Best!

更多信息，请联系我们：

地址：上海市普陀区中山北路 2911 号中关村科技大厦 1206 室

Tel: 137 6444 1515, Fax: 021-5291 8556

www.fulai-elec.com

Email: sales@fulai-elec.com